

ARM ASSIGNMENT

BOLLA VAMSIKRISHNA

bollavamsi04@gmail.com

IITH - Future Wireless Communications (FWC)

CONTENTS

I	QUESTION	1
II	COMPONENTS	1
III	TRUTH TABLE	1
	III-A LOGIC	1
IV	PROCEDURE	1
V	CONCLUSION	1

III. TRUTH TABLE

XOR gate truth table



INPUT		OUTPUT
A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0

Fig. 2. XOR GATE TRUTH TABLE

I. QUESTION

In the circuit shown below, X and Y are digital inputs, and Z is a digital output. The equivalent circuit is a

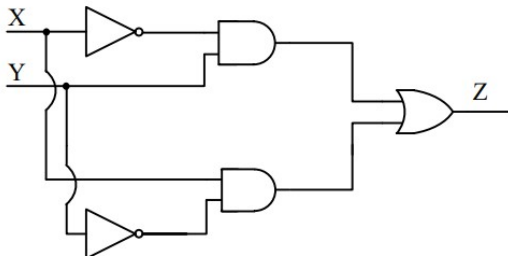


Fig. 1. CIRCUIT

A. LOGIC

From the Logic Block we get

$$Z = \overline{X}.Y + X.\overline{Y} \quad (1)$$

Which is the logic of a XOR gate

IV. PROCEDURE

- 1) Connect the anode (longer leg) of the LED to PYGMY pin 21 (on the VAMAN board.
- 2) Connect the cathode (shorter leg) of the LED to a current-limiting resistor (e.g., 220 ohms).
- 3) Connect the other end of the current-limiting resistor to the GND (ground) pin on the VAMAN.
- 4) Use PYGMY pin 22,23 on the VAMAN board to give the input manually.

V. CONCLUSION

Hence we have found the Z from digital circuit given which represents xor gate. Execute the circuit using below code.

```
https://github.com/Vamsichowdary04/Future
WirelessCommunicationFWC
-/blob/main/armvaman/src/main.c
```

II. COMPONENTS

Component	Values	Quantity
vaman	LC	1
JumperWires	M-F	10
Breadboard		1
LED		1
Resistor	220ohms	1

Table.COMPONENTS