

# FPGA ASSIGNMENT

BOLLA VAMSIKRISHNA

bollavamsi04@gmail.com

IITH - Future Wireless Communications (FWC)

## CONTENTS

<b>I</b>	<b>QUESTION</b>	1
<b>II</b>	<b>COMPONENTS</b>	1
<b>III</b>	<b>TRUTH TABLE</b>	1
III-A	LOGIC . . . . .	1
<b>IV</b>	<b>PROCEDURE</b>	1
<b>V</b>	<b>CONCLUSION</b>	1

### I. QUESTION

The output expression for the Karnaugh map shown below is.

		PQ			
		00	01	11	10
RS	00	0	1	1	0
	01	1	1	1	1
	11	1	1	1	1
	10	0	0	0	0

Fig. 1. KARNAUGH MAP

### II. COMPONENTS

Component	Values	Quantity
vaman	LC	1
JumperWires	M-F	10
Breadboard		1
LED		1
Resistor	220ohms	1

Table.COMPONENTS

### III. TRUTH TABLE

Q	R	IR	S	Q&IR S
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1

Fig. 2. TRUTH TABLE

#### A. LOGIC

From the Karnaugh map we get

$$output = Q.\bar{R} + S \quad (1)$$

### IV. PROCEDURE

- 1) Connect the anode (longer leg) of the LED to PYGMY pin 4 on the VAMAN board.
- 2) Connect the cathode (shorter leg) of the LED to a current-limiting resistor (e.g., 220 ohms).
- 3) Connect the other end of the current-limiting resistor to the GND (ground) pin on the VAMAN.
- 4) Use PYGMY pin 1,2,3 on the VAMAN board to give the input manually.

### V. CONCLUSION

Hence we have found the output from Karnaugh map given which represents  $Q\bar{R} + S$ . Execute the circuit using below code.

<https://github.com/Vamsichowdary04/FutureWirelessCommunicationFWC/blob/main/FPGAVAMAN/codes/helloworldfpga.v>